
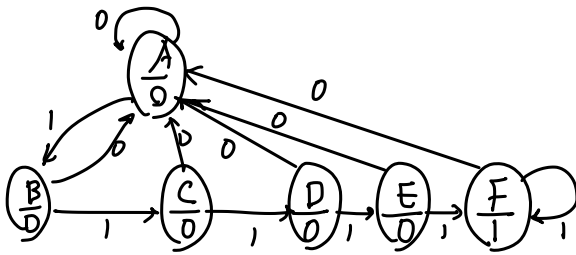


Moore Machine:

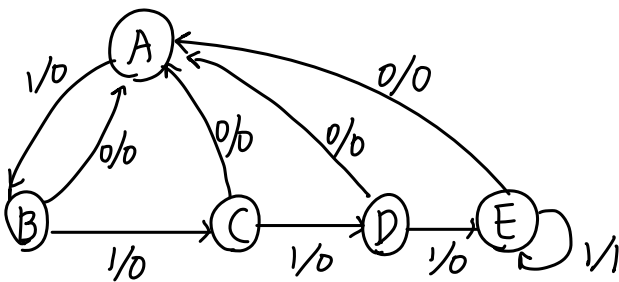

Present state	Next state		Present output
	x=0	x=1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	E	0
E	A	F	0
F	A	F	1

Mealy Machine:



q	q'		z	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	A	C	0	0
C	A	D	0	0
D	A	E	0	0
E	A	E	0	1